

Computer Architecture Lab

Logic

(Week 7)

1. Draw the circuit for Exclusive OR by using AND, OR and NOT logic gate. Exclusive OR
Equation = $A'B + AB'$

2. Draw the circuit which is capable to compare the equality of two 4-bit numbers. If equal output one, else zero.

☐ $A = A_3A_2A_1A_0$

☐ $B = B_3B_2B_1B_0$

☐ Hint: $A_0 = B_0, A_1 = B_1, A_2 = B_2, A_3 = B_3$

3. Draw the circuit which is capable to perform the addition of two 4-bit numbers. Hint: We have two 4-bits number:

☐ $\text{numA} = A_3A_2A_1A_0$

☐ $\text{numB} = B_3B_2B_1B_0$

☐ $\text{Result} = R_3R_2R_1R_0$

4. Draw the circuit which is capable of performing the subtraction of two 4-bit numbers. Hint: We have two 4-bits number

- numA = A₃A₂A₁A₀
- numB = B₃B₂B₁B₀
- Result = R₃R₂R₁R₀

5. Draw the circuit which is capable to increase the 4-bit number by 1. Like ex3, $N + 0001$.

Hint: We have two 4-bits number

□ $A = A_3A_2A_1A_0$

□ $B = 0001$

□ $R = A + B$

6. Draw the circuit which is capable to decrease the 4-bit number by 1. Like ex4, $N - 0001$. Hint: We have two 4-bits number

□ $A = A_3A_2A_1A_0$

□ $B = 0001$

□ $R = A - B$

Thanks